

6.301 Solid State Circuits

Fall Term 2010
 Problem Set 5

Issued : Oct. 8, 2010
 Due : Friday, Oct. 15, 2010


Suggested Reading: Read as many of the following as you can. All of the recommended references are on reserve at Barker Library.

1. Lundberg sections 11–18, 21 and 27.
2. Grebene sections 4 and 7.
3. Gray and Meyer sections 4.2, 6.2 and 7.3.6.


Problem 1: Current Mirrors.

For each of the following current mirrors, express I_{out}/I_{in} as a fraction of expanded polynomials in β , assuming all transistors are matched. Also, solve for the lower bound of V_{OUT} such that all transistors remain Forward Active in terms of V_{BE} and $V_{CE,sat}$. You cannot neglect base currents.


(i) Improved Current Mirror:

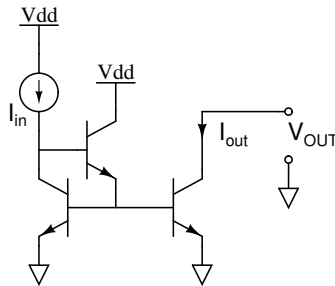


(ii) Cascode Current Mirror:

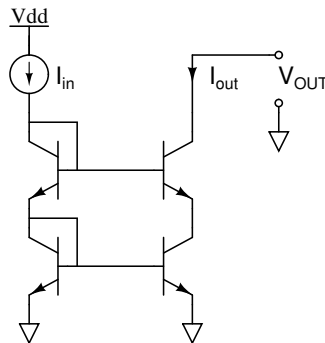

(iii) Improved Wilson Current Mirror:

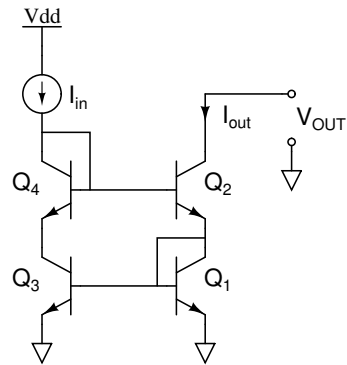


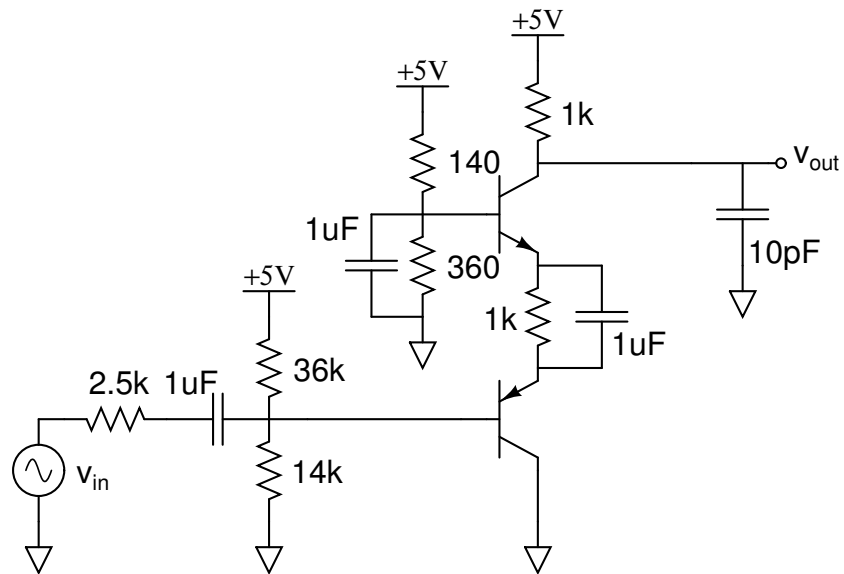Problem 2: The following amplifier is in a stacked Emitter-Follower, Common-Base configuration. Assume $V_{BE,on}=0.6\text{V}$, $c_{\mu}=2\text{pF}$, $c_{\pi}=20\text{pF}$, $\beta_{npn}=200$ and $\beta_{pnp}=100$. You may neglect r_b and r_o .




- Calculate the midband small-signal gain.
- Using the OCT method, estimate the upper -3dB frequency.
- Using the SCT method, estimate the lower -3dB frequency.

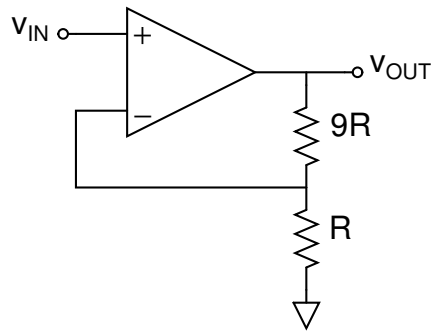
Problem 3: Operational Amplifiers. Consider the following non-inverting configuration:



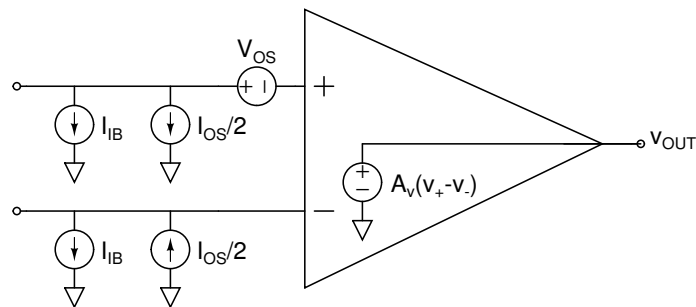We know that practical op amp circuits do not implement “ideal op amp” behavior. This is the op amp equivalent circuit including Input Offset Voltage V_{OS} , Input Bias Current I_{IB} , Input Offset Current I_{OS} , and Finite Gain A_V :



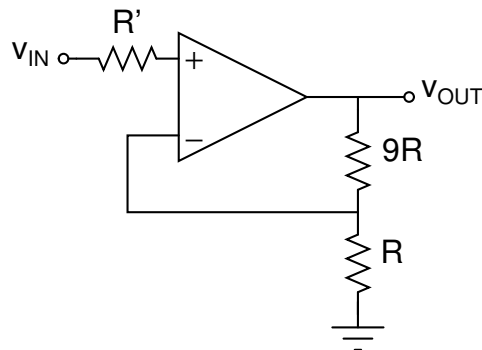- (a) For the non-inverting op amp configuration, solve v_{OUT} in terms of v_{IN} and the following non-idealities.
- (i) Input Offset Voltage V_{OS} (assuming no I_{IB} or I_{OS} ; and infinite gain)
 - (ii) Input Bias Current I_{IB} (assuming no V_{OS} or I_{OS} ; and infinite gain)
 - (iii) Input Offset Current I_{OS} (assuming no V_{OS} or I_{IB} ; and infinite gain)
 - (iv) Finite Gain A_V (assuming no V_{OS} , I_{IB} or I_{OS})
- (b) It is possible to counteract the dependence on I_{IB} found in part (a-ii) with a resistor in series with the non-inverting terminal. Find the value of R' which eliminates the dependence on I_{IB} found in part (a-ii).



MIT OpenCourseWare
<http://ocw.mit.edu>

6.301 Solid-State Circuits
Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.