

MITOPENCOURSEWARE
MASSACHUSETTS INSTITUTE OF TECHNOLOGY

6.776

High Speed Communication Circuits

Lecture 6





MOS Transistors, Passive Components, Gain-Bandwidth Issue for Broadband Amplifiers

Massachusetts Institute of Technology


February 17, 2005

Copyright © 2005 by Hae-Seung Lee and Michael H. Perrott

    Basics of MOS Large Signal Behavior (Qualitative)



 
Basics of MOS Large Signal Behavior (Quantitative)



$$I_D = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T - V_{DS}/2) V_{DS}$$


for $V_{DS} \ll V_{GS} - V_T$
 
$$I_D \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) V_{DS}$$



$$\Delta V = V_{GS} - V_T$$
 
$$\Delta V = \sqrt{\frac{2I_D L}{\mu_n C_{ox} W}}$$




$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

(where λ corresponds to channel length modulation)

Analysis of Amplifier Behavior

 - Typically focus on small signal behavior
 - Work with a linearized model such as hybrid- π
- To do small signal analysis:




Small Signal Analysis Steps


- 1) Solve for bias current I_D
- 2) Calculate small signal parameters (such as g_m , r_o)
- 3) Solve for small signal response using transistor hybrid- π small signal model

MOS DC Small Signal Model

- Assume transistor in saturation:

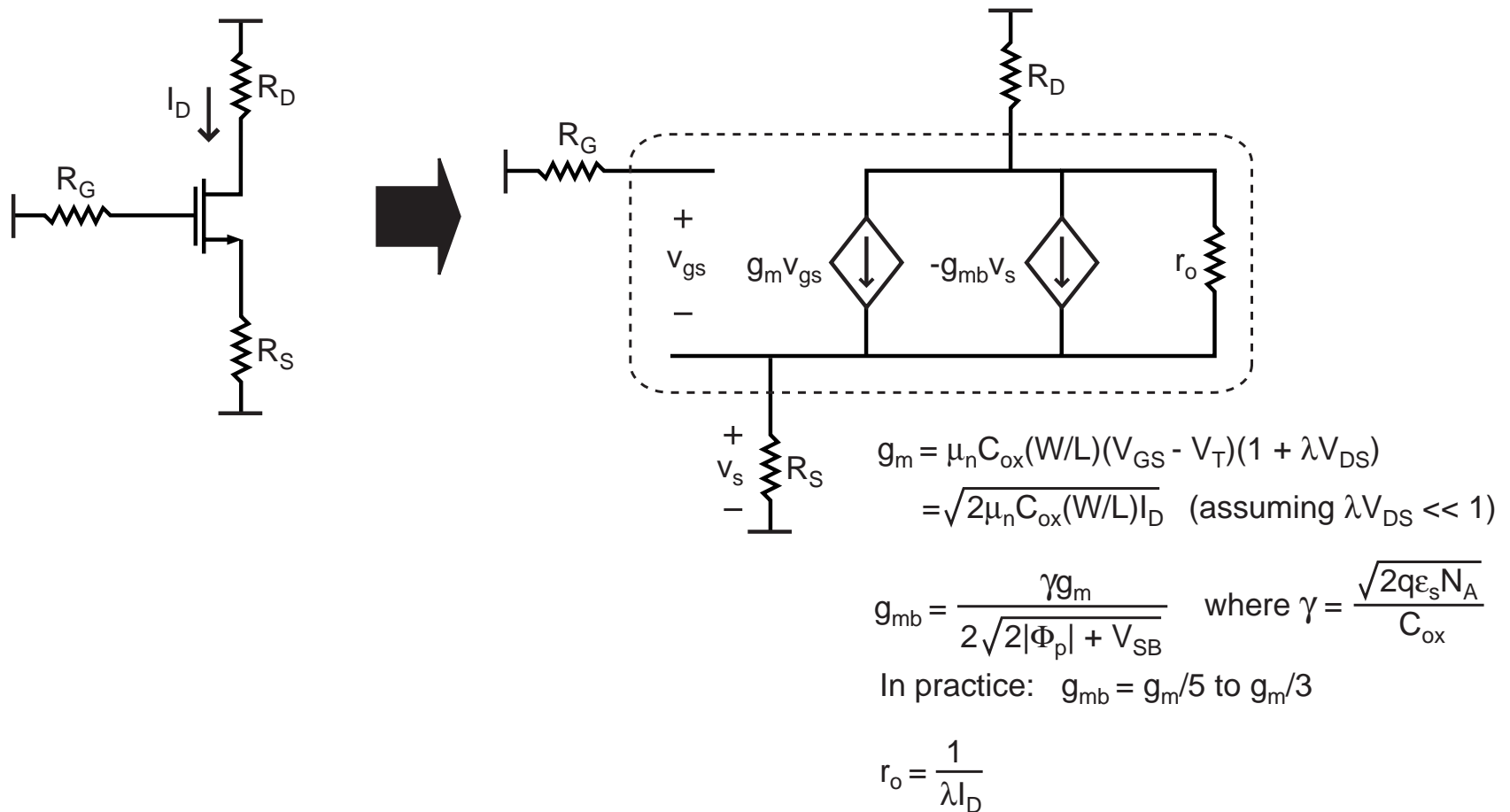

Capacitors For MOS Device In Saturation

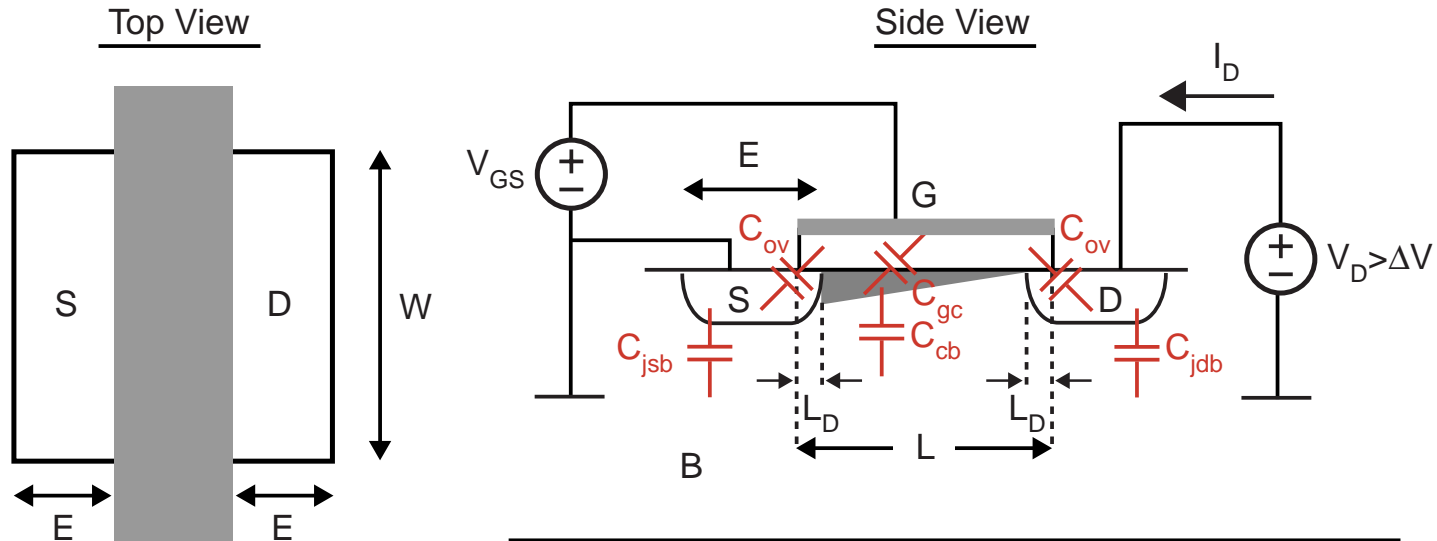

junction bottom wall
cap (per area)

junction sidewall
cap (per length)

$$\text{source to bulk cap: } C_{\text{j\text{sb}}} = \frac{C_j(0)}{\sqrt{1 + V_{\text{SB}}/|\Phi_B|}} WE + \frac{C_{\text{j\text{sw}}}(0)}{\sqrt{1 + V_{\text{SB}}/|\Phi_B|}} (W + 2E)$$


(make $2W$ for "4 sided" perimeter in some cases)

$$\text{drain to bulk cap: } C_{\text{j\text{db}}} = \frac{C_j(0)}{\sqrt{1 + V_{\text{DB}}/|\Phi_B|}} WE + \frac{C_{\text{j\text{sw}}}(0)}{\sqrt{1 + V_{\text{DB}}/|\Phi_B|}} (W + 2E)$$

$$\text{overlap cap: } C_{\text{ov}} = WL_D C_{\text{ox}} + WC_{\text{fringe}} \quad \text{gate to channel cap: } C_{\text{gc}} = \frac{2}{3} C_{\text{ox}} W(L - 2L_D)$$

channel to bulk cap: C_{cb} - ignore in this class

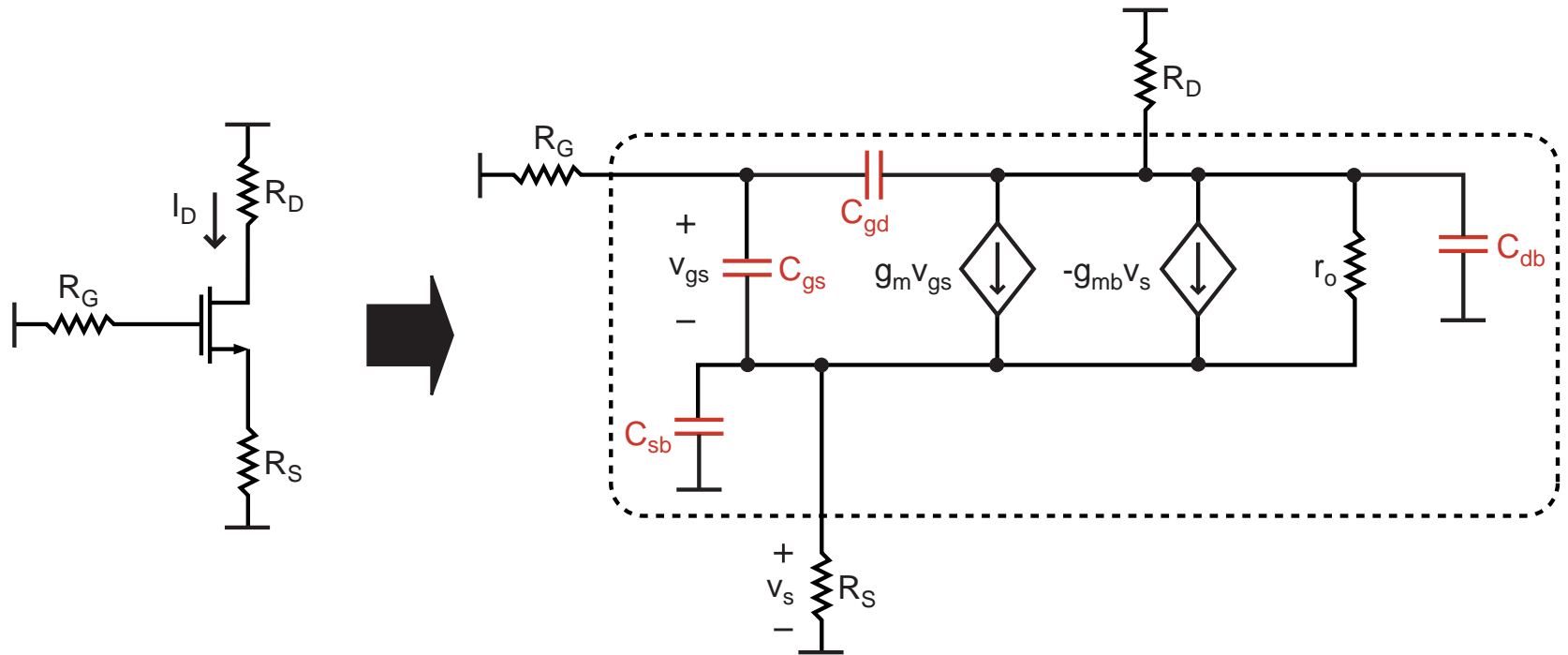MOS AC Small Signal Model (Device in Saturation)



$$C_{gs} = C_{gc} + C_{ov} = \frac{2}{3} C_{ox} W(L-2L_D) + C_{ov}$$

$$C_{gd} = C_{ov}$$

$$C_{sb} = C_{jsb} \quad (\text{area + perimeter junction capacitance})$$

$$C_{db} = C_{jdb} \quad (\text{area + perimeter junction capacitance})$$

Wiring Parasitics

■ Capacitance

- Gate: cap from poly to substrate and metal layers
- Drain and source: cap from metal routing path to substrate and other metal layers

■ Resistance

- Gate: poly gate has resistance (reduce by silicide) long metal lines can add resistance
- Drain and source: some resistance in diffusion region (reduce by silicide), and from routing long metal lines

■ Inductance


- Gate: poly gate has negligible inductance, but long wires can add inductance
- Drain and source: becomes an issue for long wires

Extract these parasitics from circuit layout

Frequency Performance of a CMOS Device


- **Two figures of merit in common use**
 - f_t : frequency for which current gain is unity
 - f_{\max} : frequency for which power gain is unity
- **Common intuition about f_t**
 - **Gain, bandwidth product is conserved**
 - $\Rightarrow \text{Gain} \cdot \text{Bandwidth} = f_t$
 - **We will see that MOS devices have an f_t that is a function of bias**
 - This effect strongly impacts high frequency amplifier topology selection

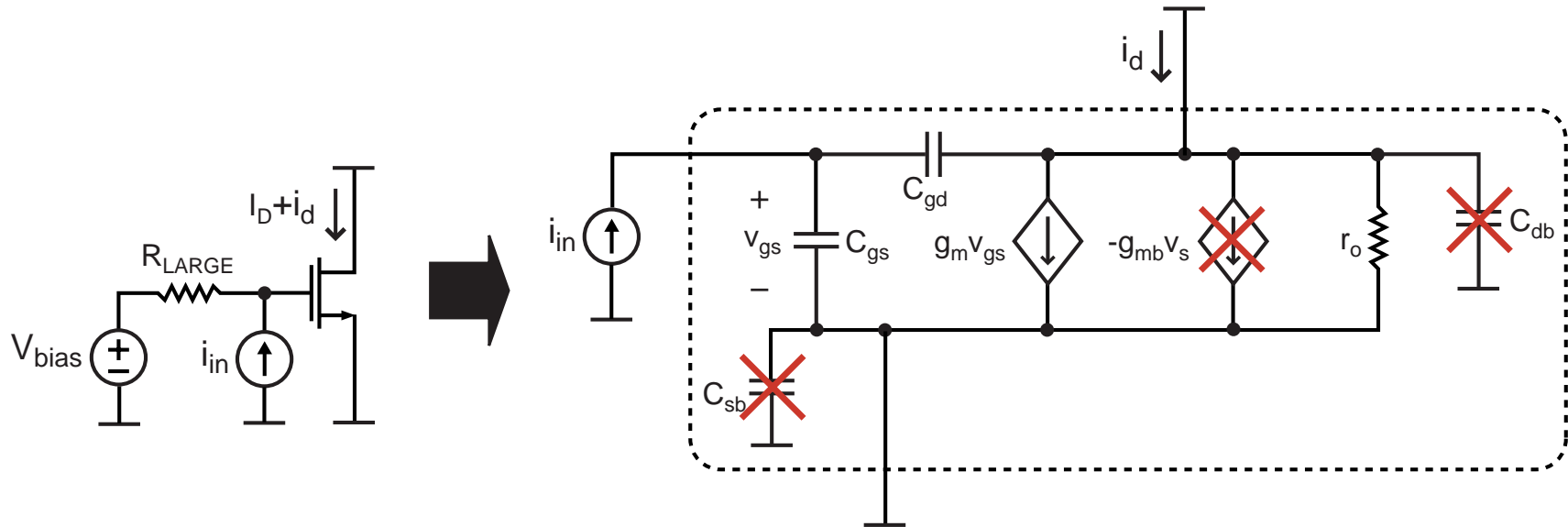Derivation of f_t for MOS Device in Saturation



- Assumption is that input is current, output of device is short circuited to a supply voltage
 - Note that voltage bias is required at gate
 - The calculated value of f_t is a function of this bias voltage

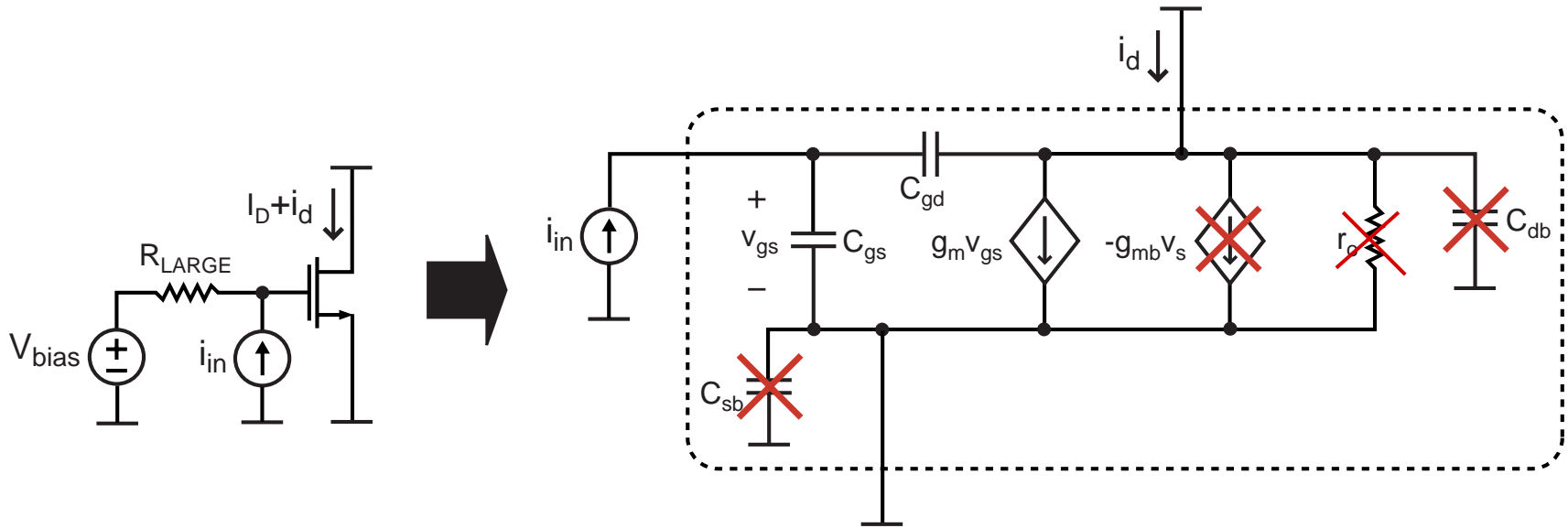
Derivation of f_t for MOS Device in Saturation



$$i_d = g_m v_{gs} = g_m \left(\frac{1}{s(C_{gs} + C_{gd})} \right) i_{in}$$

$$\Rightarrow \frac{i_d}{i_{in}} = \frac{g_m}{j\omega(C_{gs} + C_{gd})}$$

 Derivation of f_t for MOS Device in Saturation



$$\omega_t = \frac{g_m}{C_{gs} + C_{gd}}$$

$$\Rightarrow f_t = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$i_d = g_m v_{gs} = g_m \left(\frac{1}{s(C_{gs} + C_{gd})} \right) i_{in}$$

$$\Rightarrow \frac{i_d}{i_{in}} = \frac{g_m}{j\omega(C_{gs} + C_{gd})}$$

Why is f_t a Function of Voltage Bias?

$$f_t = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

- f_t is a ratio of g_m to gate capacitance
 - g_m is a function of gate bias, while gate cap is not (in strong inversion)
- First order relationship between g_m and gate bias:

$$g_m \approx \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t)$$

- The larger the gate bias, the higher the value for f_t
- Alternately, f_t is a function of current density

$$\frac{g_m}{C_{gs} + C_{gd}} \approx \frac{\sqrt{2\mu_n C_{ox} (W/L) I_d}}{(2/3)WLC_{ox} + W(C_{ov}/W)} \propto \sqrt{\frac{I_d}{W}} \frac{1}{L^{3/2}}$$

- So f_t maximized at max current density (and minimum L)

Unity Power Gain Frequency f_{max}

From pages 176-178 (2nd ed.) 70-72 (1st ed.) of text book
for derivation on f_{max}

$$\omega_{max} \approx \frac{1}{2} \sqrt{\frac{\omega_T}{r_g C_{gd}}}$$

- r_g is the series parasitic gate resistance
- f_{max} can be much higher than f_T : make gate resistance small (by careful layout)
- Output capacitance has no effect (can be tuned out by inductor)

Speed of NMOS Versus PMOS Devices

$$f_t = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

- **NMOS devices have much higher mobility than PMOS devices (in typical bulk CMOS processes)**

$$\mu_n \approx 2.5\mu_p \quad \text{for many processes}$$

$$\Rightarrow f_t \text{ of NMOS} \approx 2.5 \times f_t \text{ of PMOS}$$


- **NMOS devices provide approximately $2.5 \times g_m$ for a given amount of capacitance and gate bias voltage**
- **Also, NMOS devices provide approximately $2.5 \times I_d$ for a given amount of capacitance and gate bias voltage**

Integrated Passive Components for RF Circuits

- We will only consider passive components appropriate for RF use
- High Q, low parasitics, and good linearity are generally desired (bias circuit is an exception)
- Well resistors, diffused resistors, poly-n+ capacitors even poly-poly capacitors do not perform very well in these regards

Polysilicon Resistors

 - Use unsilicided polysilicon to create resistor



- Key parameters

- Resistance (usually 100- 200 Ohms per square)
- Parasitic capacitance (usually small)
 - Appropriate for high speed amplifiers
- Linearity (excellent)
- Accuracy (usually can be set within $\pm 15\%$)

MOS Resistors

- Bias a MOS device in its triode region




$$R_{ds} \approx \frac{1}{\mu C_{ox} W/L ((V_{gs} - V_T) - V_{DS})}$$

- High resistance values can be achieved in a small area (MegaOhms within tens of square microns)
- Parasitic capacitance is large (gate capacitance!)
- Resistance is quite nonlinear
 - Appropriate for small swing circuits or DC (bias) circuits

High Density Capacitors (Biasing, Decoupling)

 
- MOS devices offer the highest capacitance per unit area
 - Voltage must be high enough to invert the channel



- Key parameters
 - Capacitance value
 - Raw cap value from MOS device is about 8-8.5 fF/ μ^2 for 0.18u CMOS
 - Q (i.e., amount of series resistance)
 - Maximized with minimum L (tradeoff with area efficiency)

MOS Capacitors, Cnt'd

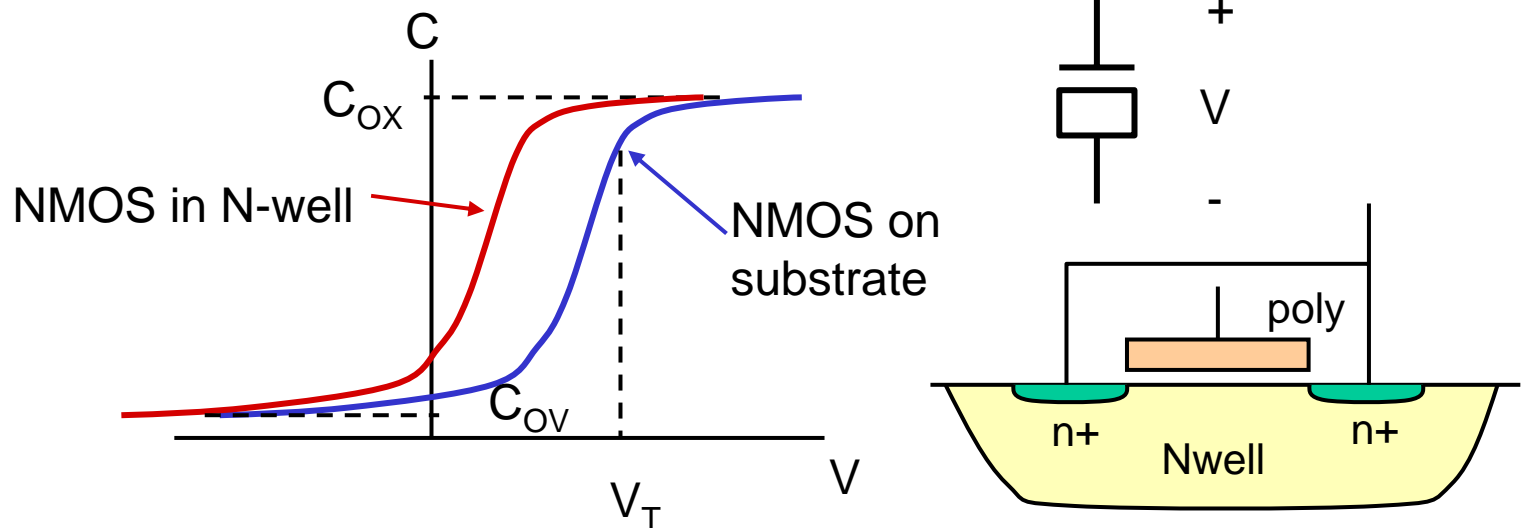
- Putting NMOS capacitor in NWell allows operation at lower voltage



- The non-linearity is often exploited in VCO designs as varactors


High Q Capacitors (Signal Path)

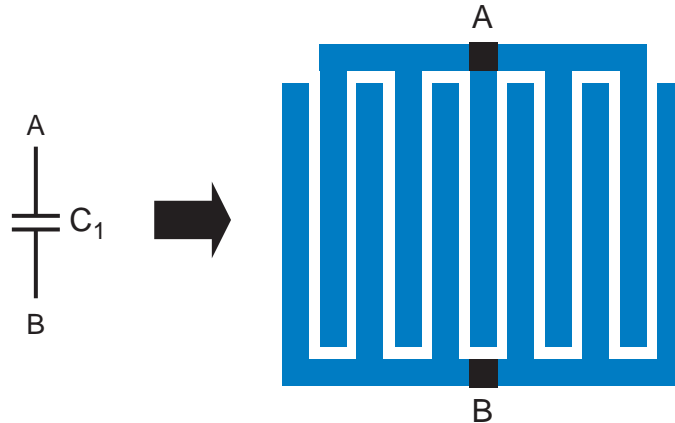- Lateral metal capacitors offer high Q and reasonably large capacitance per unit area
 - Stack many levels of metal on top of each other (best layers are the top ones), via them at maximum density



- Accuracy often better than $\pm 10\%$
- Parasitic cap is symmetric, typically less than 10% of cap value

Stacked Lateral Flux Capacitor

 

■ **Example:** $C_T = 1.5 \text{ fF}/\mu\text{m}^2$ for $0.24\mu\text{m}$ process with 7 metals, $L_{\min} = W_{\min} = 0.24\mu\text{m}$, $t_{\text{metal}} = 0.53\mu\text{m}$

■ See “Capacity Limits and Matching Properties of Integrated Capacitors”, Aparicio et. al., JSSC, Mar 2002

Fractal Capacitor

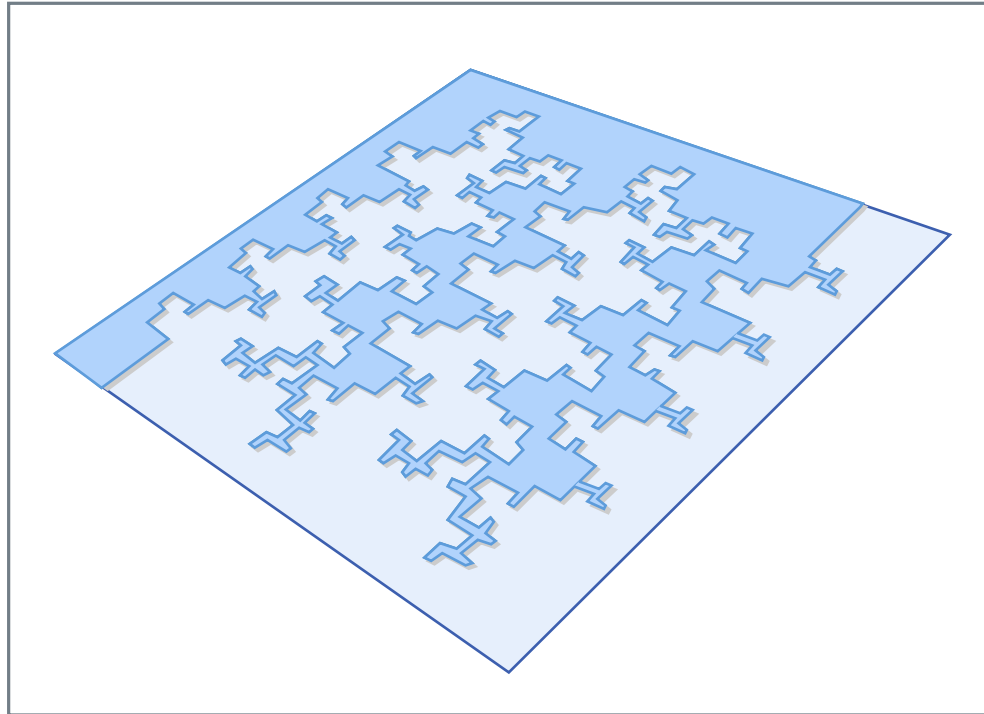



Figure by MIT OCW.

- **Maximizes perimeter area: up to 10x increase in unit capacitance**
- **Limited by lithography**

See A. Shanhani et. al., “A 12 mW, Wide Dynamic Range CMOS Front-End Circuit for Portable GPS Receiver,” Digest of Technical Papers, ISSCC 1997

Spiral Inductors

 
- Create integrated inductor using spiral shape on top level metals (may also want a patterned ground shield)



- Key parameters are Q (< 10), L (1-10 nH), self resonant freq.
- Usually implemented in top metal layers to minimize series resistance, coupling to substrate
- See using Mohan et. al, "Simple, Accurate Expressions for Planar Spiral Inductances, JSSC, Oct, 1999, pp 1419-1424
- Verify inductor parameters (L , Q , etc.) using ASITIC
<http://formosa.eecs.berkeley.edu/~niknejad/asitic.html>

Bondwire Inductors


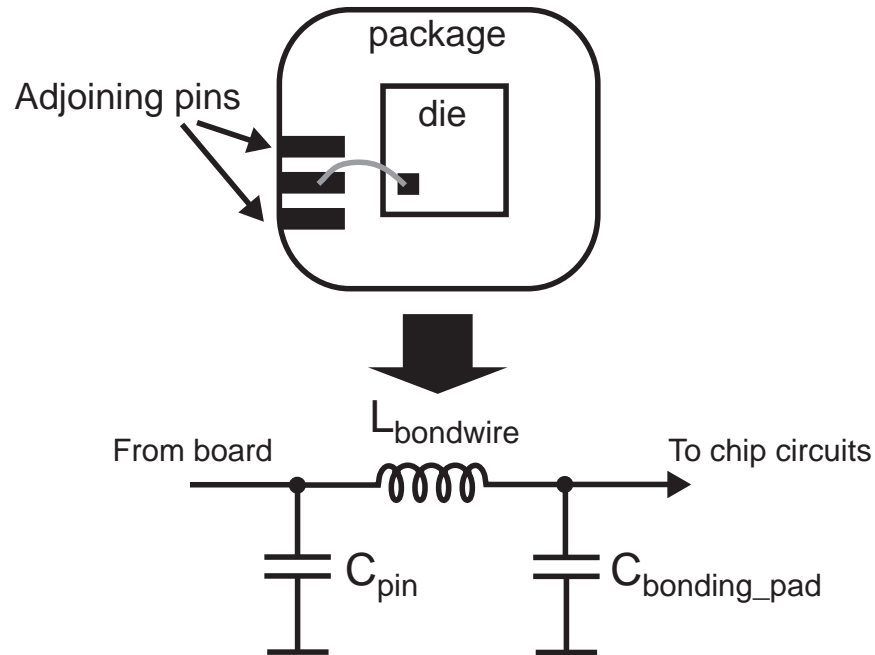
- Used to bond from the package to die
 - Can be used to advantage



- Properties
 - Inductance (≈ 1 nH/mm – usually achieve 1-5 nH)
 - Inductance value is difficult to control (chip-package alignment, bondwire height, etc.)
 - Q (much higher than spiral inductors – typically > 40)

Integrated Transformers

  - Utilize magnetic coupling between adjoining wires



- Key parameters


- L (self inductance for primary and secondary windings)
- k (coupling coefficient between primary and secondary)

Note: $k = \frac{M}{\sqrt{L_1 L_2}}$ where $M =$ mutual inductance

- Design – ASITIC, other CAD packages

High Speed Transformer Example – A T-Coil Network

 - A T-coil consists of a center-tapped inductor with mutual coupling between each inductor half




- Used for bandwidth enhancement
 - See S. Galal, B. Ravazi, “10 Gb/s Limiting Amplifier and Laser/Modulator Driver in 0.18u CMOS”, ISSCC 2003, pp 188-189 and “Broadband ESD Protection ...”, pp. 182-183

Broadband Amplifiers

High Frequency, Broadband Amplifiers

 
- The first thing that you typically do to the input signal is amplify it



- **Function**
 - Boosts signal levels to acceptable values
 - Provides reverse isolation
- **Key performance parameters**
 - Gain, bandwidth, noise, linearity

Gain-bandwidth Trade-off

- Common-source amplifier example

 

C_{tot} : total capacitance at output node


DC gain $A = g_m R_L$

3 dB bandwidth $\omega_h = \frac{1}{R_L C_{tot}}$

Gain-bandwidth $GB = \frac{g_m}{C_{tot}}$

Gain-bandwidth Trade-off

- Common-source amplifier example

 

- Given the 'origin pole' g_m/C_{tot} , higher bandwidth is achieved only at the expense of gain
- The 'origin pole' g_m/C_{tot} must be improved for better GB

Gain-bandwidth Improvement

- How do we improve g_m/C_{tot} ?
- Assume that amplifier is loaded by an identical amplifier and fixed wiring capacitance is negligible
- Since $g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$ and $C_{tot} \propto W$
$$\frac{g_m}{C_{tot}} \propto \frac{V_{GS} - V_T}{L}$$
- To achieve maximum GB in a given technology, use minimum gate length, bias the transistor at maximum $V_{GS} - V_T$
- When velocity saturation is reached, higher $V_{GS} - V_T$ does not yield higher g_m
- In case fixed wiring capacitance is large, power consumption must be also considered

Gain-bandwidth Observations

- **Constant gain-bandwidth is simply the result of single-pole roll off – it's *not* fundamental!**
- **It implies a single-pole frequency response may not be the best for obtaining gain and bandwidth simultaneously**
- **Single-pole roll off is necessary for some circuits, e.g. for stability, but not for broad-band amplifiers**