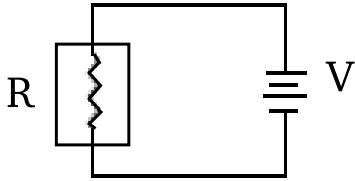



8.022 Lecture Notes Class 31 - 11/13/2006



$$V = IR \quad \underline{\text{Macroscopic Ohm's Law}}$$

$$\Sigma \Delta V \quad \underline{\text{Kirchoff's I}}$$
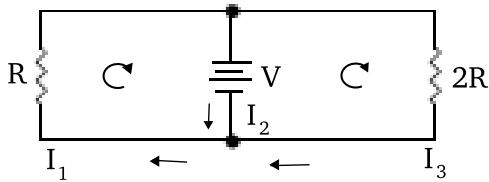
$$\iff \oint \vec{E} \cdot d\vec{l} = 0$$




Three loops but only two interesting ones.

Charge is conserved at junctions.

$$\Sigma I = 0 \quad \underline{\text{Kirchoff's II}}$$

### Resistors in Series

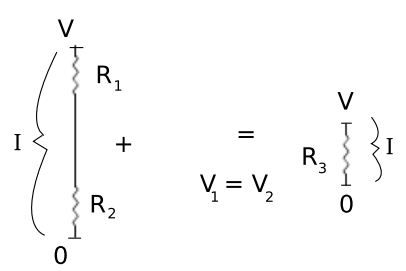


Use  $\Sigma V = 0$

$$V_1 + V_2 = V$$

$$R = \frac{V}{I} = \frac{V_1 + V_2}{I} = \frac{V_1}{I} + \frac{V_2}{I} = R_1 + R_2$$


### Resistors in Parallel

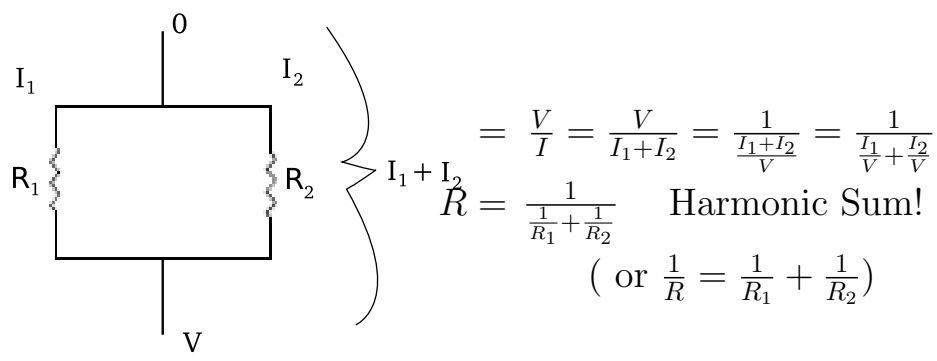

$$R = \frac{V}{I_1 + I_2} = \frac{1}{\frac{I_1 + I_2}{V}} = \frac{1}{\frac{I_1}{V} + \frac{I_2}{V}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$


Harmonic Sum!  
( or  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$  )

### Capacitors in Series

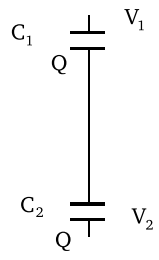


$$C = \frac{Q}{V} = \frac{Q}{V_1 + V_2} = \frac{1}{\frac{V_1}{Q} + \frac{V_2}{Q}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

### Capacitors in Parallel

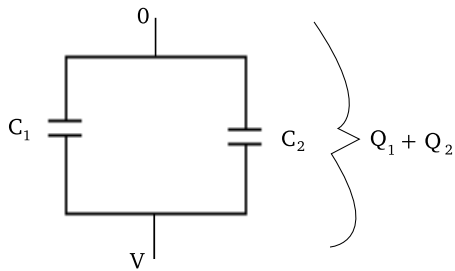

$$C = \frac{Q_1 + Q_2}{V} = \frac{Q_1}{V} + \frac{Q_2}{V} = C_1 + C_2$$

### Resistor Cube

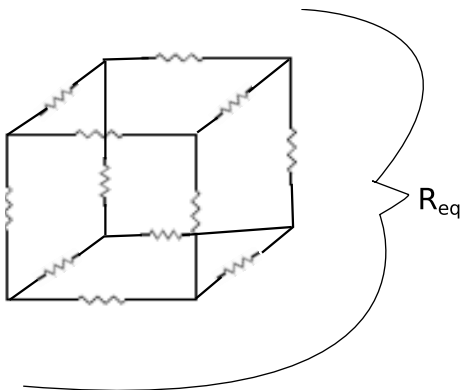

$$\begin{aligned}\frac{1}{R_{\text{eq}}} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{R + \frac{1}{\frac{1}{2R} + \frac{1}{2R}}} + \frac{1}{R + \frac{1}{\frac{1}{2R} + \frac{1}{2R}}} + \frac{1}{R + \frac{1}{\frac{1}{2R} + \frac{1}{2R}}} \\ &= \frac{3}{R+R} \\ &= \frac{3}{2R} \\ R_{\text{eq}} &= \frac{2}{3}R\end{aligned}$$